

# ANODE

**Inside this issue:**

Editor's Comments	1
A Collection of Circuit Ideas	1

## Editor's Comments

**Volume 10, Issue 5  
November 2009**

<http://www.amateurradio.org.za/>

**As Promised**

In this issue I am going to fill it with "Circuit Ideas".

**62,000 broadband customers desert Tiscali**

The company has claimed the departures were anticipated, and says its new "customer retention scheme" has improved confidence in the service and slowed departures, ahead of the deal's finalisation.

**Lessons in Electronics**

<http://www.openbookproject.net/electricCircuits/>

**South African Amateur Radio Development Trust**

**Don't Mess with Seniors**

*(continued on page 9)*

## A Collection of Circuit Ideas - 1

**One-shot timer circuit**

The circuit shown is a four-transistor configuration which is similar in operation to the well-known 555 device but, since the normal state is all transistors on, the circuit has a high de-

gree of impulse noise immunity - thereby avoiding the occurrence of spurious timing cycles which are sometimes troublesome in i.c. timing circuits.


In operation, the voltage on the timing capacitor C rises until Tr2 begins to conduct which in turn causes Tr 3, Tr 4 and Tr, also to switch on. Regeneration in the circuit is caused by the interaction of Tr 2 and Tr 4, and the timing capacitor is discharged to about 0.6V by the operation of Tr 3 and Tr 1. The timing cycle is initiated either by the application of VCC or by the opening of Sp As in the 555, the timing period is Vcc independent as long as it is stable during the timing cycle.

J . L. Linsley Hood, Taunton, Somerset.

Contributors to Circuit Ideas are  
*(continued on page 2)*

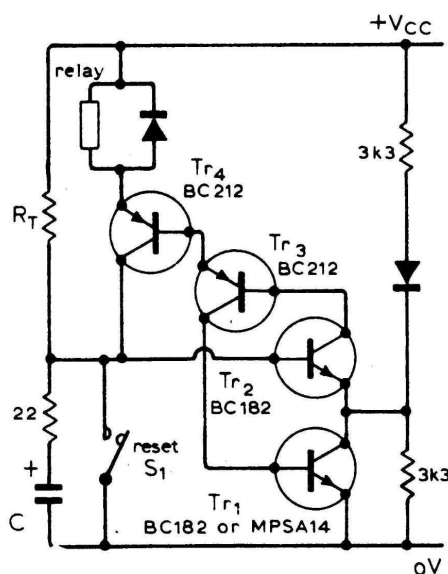**Special points of interest:**

- Contact details on back page (corrected & updated)
- Ham-Comp Latest on web site.




## A Collection of Circuit Ideas - 1

(continued from page 1)

urged to say what is new or improved about their circuit early in the item, preferably in the first sentence.

can be easily modified for different voltages by changing the zener diodes.

S. C. Mathur Weybridge Surrey

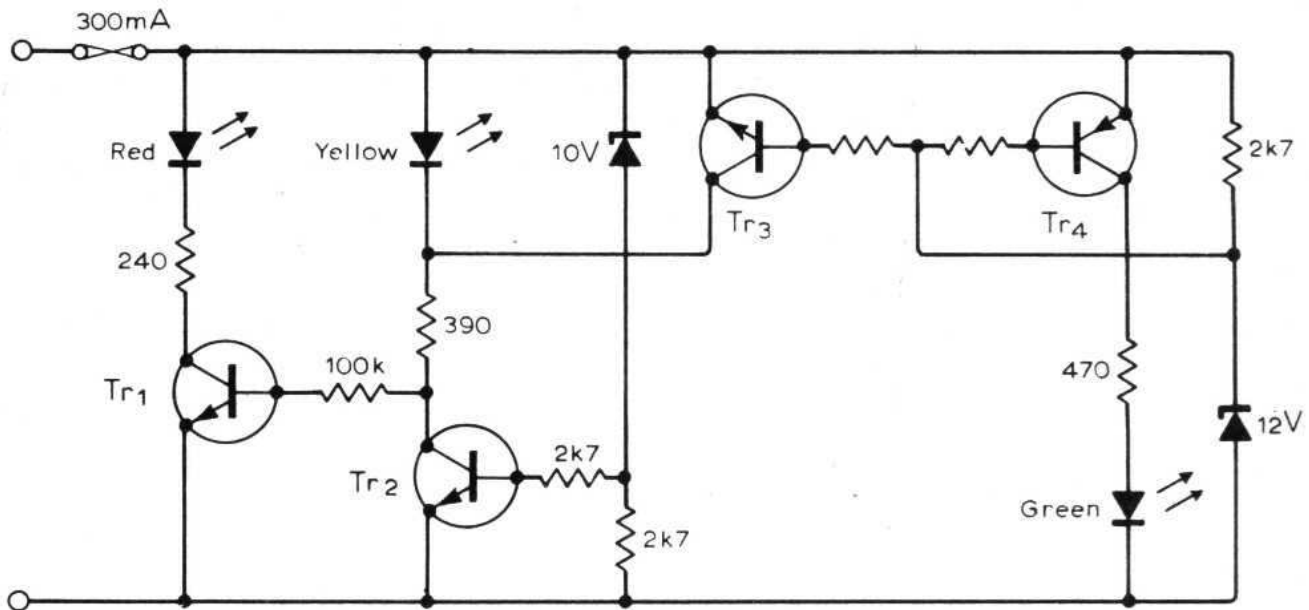

### Automotive voltage indicator

An indication of battery voltage is useful to the motorist for monitoring the battery's capacity to delivery current, and as a check on the efficiency of the dynamo or alternator. This circuit is a solid-state alternative to a moving coil meter. The table shows the outputs obtained over the critical range of 10 to 14V.

When the input is below 10V, Tr 2, Tr 3, and Tr 4 are off and Tr 1 is turned on. As the voltage rises the 10V zener diode begins to conduct, Tr 2 receives base current and turns Tr1 off.

At approximately 11V both Tr 1, and Tr 2 are on, but at 12V only. Tr 2 is on. Similarly, Tr 4 is turned on-as the voltage rises to 14V and the 12V zener conducts.

Transistor Tr 3 takes current from the yellow L.e.d. and turns it off while Tr 2 remains in conduction to keep the red L.e.d. off. The circuit

### Bench power supply


The circuit shown provides 0 to 15V and a current up to 175 mA. Current limiting is provided by the 5.6-ohm. resistance and the diode D1. When the voltage across the 5.6-ohm resistance exceeds about 1.2V, the current source TY, produces less current and the output voltage is reduced.

The 15-k Ohm resistor from the emitter of Tr 1 provides feedback so as to reduce the current variations through the regulator diode. A 10% line voltage change therefore produces only a 2 mV + 0.0 1% change in  $V_{out}$ . A full load current change produces a 1.5 mV output voltage change; and the output voltage recovers in 3 ps to within 10 mV of  $V_{out}$  after a full load -current change. The three-transistor combination TY29

(Continued on page 3)


# A Collection of Circuit Ideas - 1

(Continued from page 2)

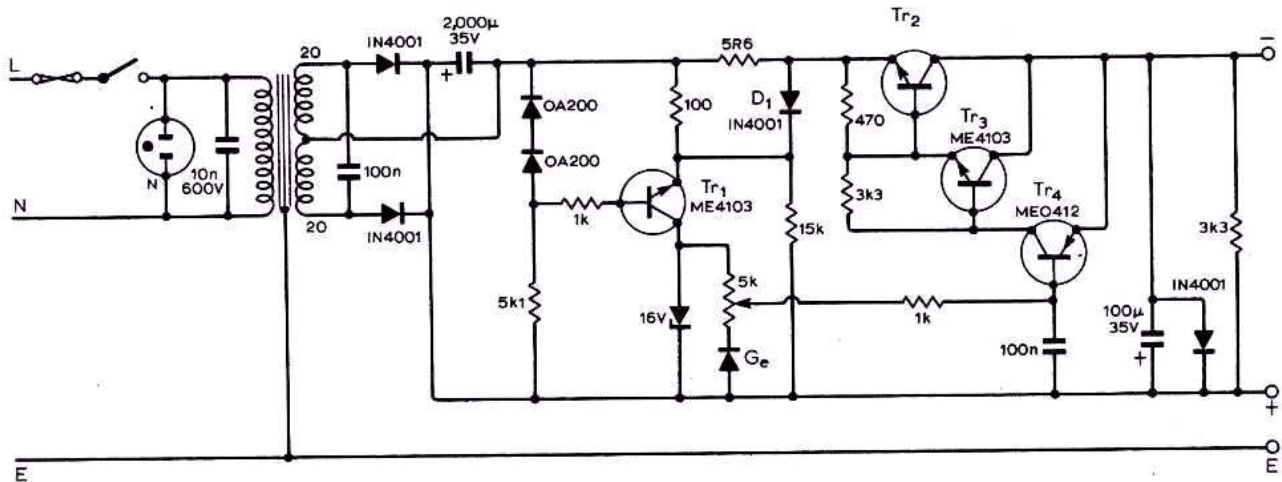

Tr<sub>1</sub> and Tr<sub>2</sub>, therefore provides fairly high gain and wide bandwidth. Output impedance at 100 kHz is less than 0.3 ohm. Output voltage temperature coefficient depends on the regulator diode temperature coefficient, the base-emitter junction of Tr<sub>1</sub> and, at, low voltage, the germanium diode. In this respect the circuit is inferior to conventional circuits and a coefficient of  $12\text{mV} \pm 0.10/6/\text{deg C}$  is achieved. Output ripple voltage is greatly dependent on the Early effect in Tr<sub>4</sub>. Using the device shown a ripple of less than 1 mV is obtained. Charge storage spikes from the rectifier diodes are removed by the 100 nF capacitor across the transformer secondary.

J. A. Roberts, Merthyr Tydfil.

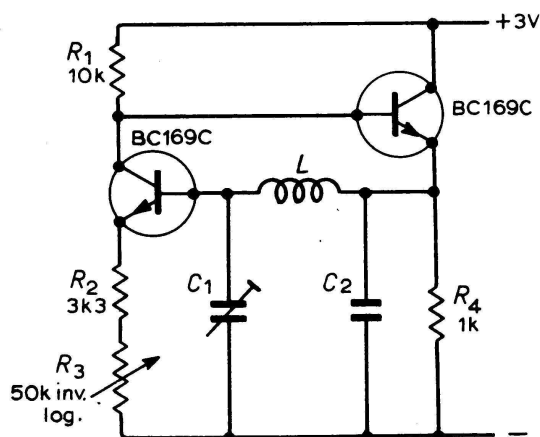

## Good-tempered LC oscillator


Transistor oscillator circuits are prone to the Vices of squegging, operating at the wrong frequency, or just failing to oscillate if used in conjunction with "unsuitable" inductors or capacitors in the tuned circuit. The arrangement illustrated was derived from the Colpitts circuit to provide a simple way of checking the inductance of a collection of iron-cored inductors, but it can be used as a general-purpose oscillator circuit up to about 10 MHz. Feedback is negative at all frequencies at which the LC network does not provide phase inversion and voltage step-up, and the only time-constant is the inevitable one introduced by the tuning components and

(continued on page 4)
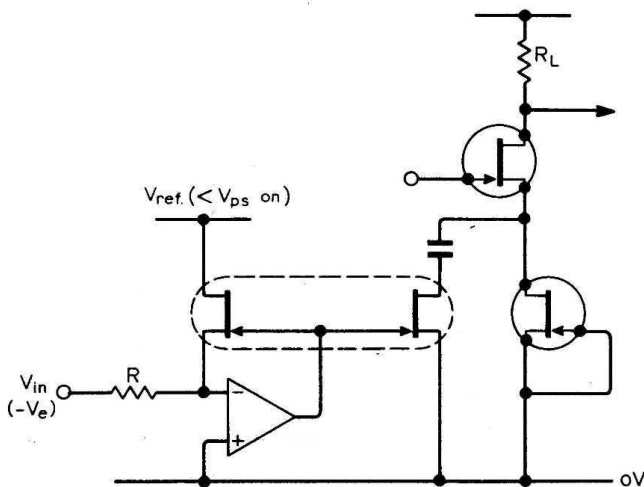
# A Collection of Circuit Ideas - 1

(Continued from page 3)


associated resistances. Capacitances C1 and C2 are effectively in series, and it is possible to make C2 much greater than C1 and so avoid curtailment of the tuning range. If waveform is un-



## Linear Voltage Controlled Amplifier

This circuit is based on dual matched f.e.t.'s. and can be used in applications such as linear voltage controlled amplifiers and two-quadrant multipliers. The resistance of the f.e.t. in the feedback loop is adjusted automatically to source the current demanded by  $V_i$ . This resistance, and therefore the resistance of the other f.e.t., varies inversely with input voltage. The gain of the amplifier stage is given by  $R_L/V_{ref} * V_i$ , and is variable over about 80 dB.

B. Turneir & J. Custo, Tewkesbury, Glos.

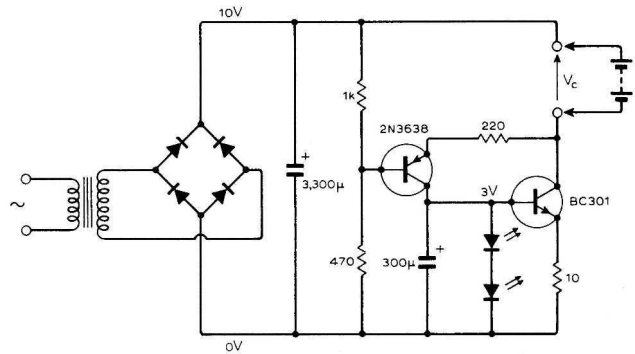

## Battery charger


The simple circuit shown is for charging four size D nickel cadmium cells in series at constant current and with automatic voltage limiting. The BC301 acts as a current source, its base voltage being stabilized at about 3V by two l.e.d's, which may also be used to indicate the charge condition. The 2N3638 provides voltage limiting by cutting off the BC301 when  $V_c$  approaches the voltage across the 1 kg. branch of the voltage divider. For the component values shown, charge current is 260 mA at low  $V_c$ , 200 mA at  $V_c$  of 5V, and decreases to virtually zero at  $V_c$  of 6.5V.

N. H. Sabah, American University, Beirut.

(Continued on page 5)

# A Collection of Circuit Ideas - 1

(Continued from page 4)

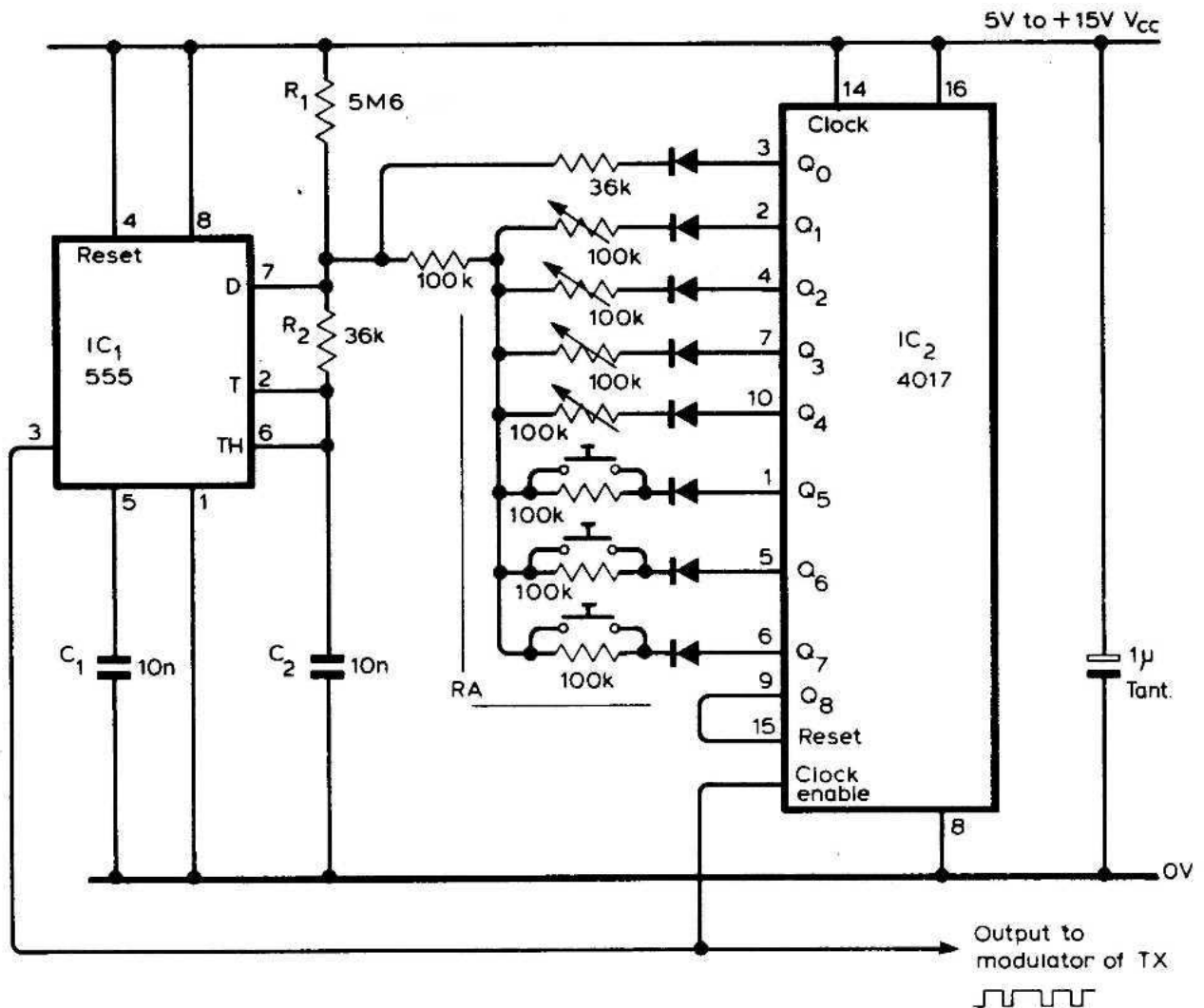

## radio control encoder

A simple seven-channel radio control encoder can be built with two ICs as shown. The circuit operates from 5 to 15 V at 2.5 to 5 mA and will provide an output current of up to 200 mA. The 555 is used in the astable mode with an off time of 0.25 ms and an on time between 1 and 2 ms except for channel 0 which produces a 0.5 ms sync. pulse.

The decade counter is clocked by the falling edge of the output and is reset when Q8 goes high. Resistor R1 ensures that the 555 oscillates


at a low frequency if no outputs are selected. If proportional control is not required, resistors RA can be fixed values. For a supply below 8V a Zener regulator should be used to prevent variations in pulse width.

S. Ingham Moseley Birmingham

(continued on page 6)

## A Collection of Circuit Ideas - 1

(continued from page 5)

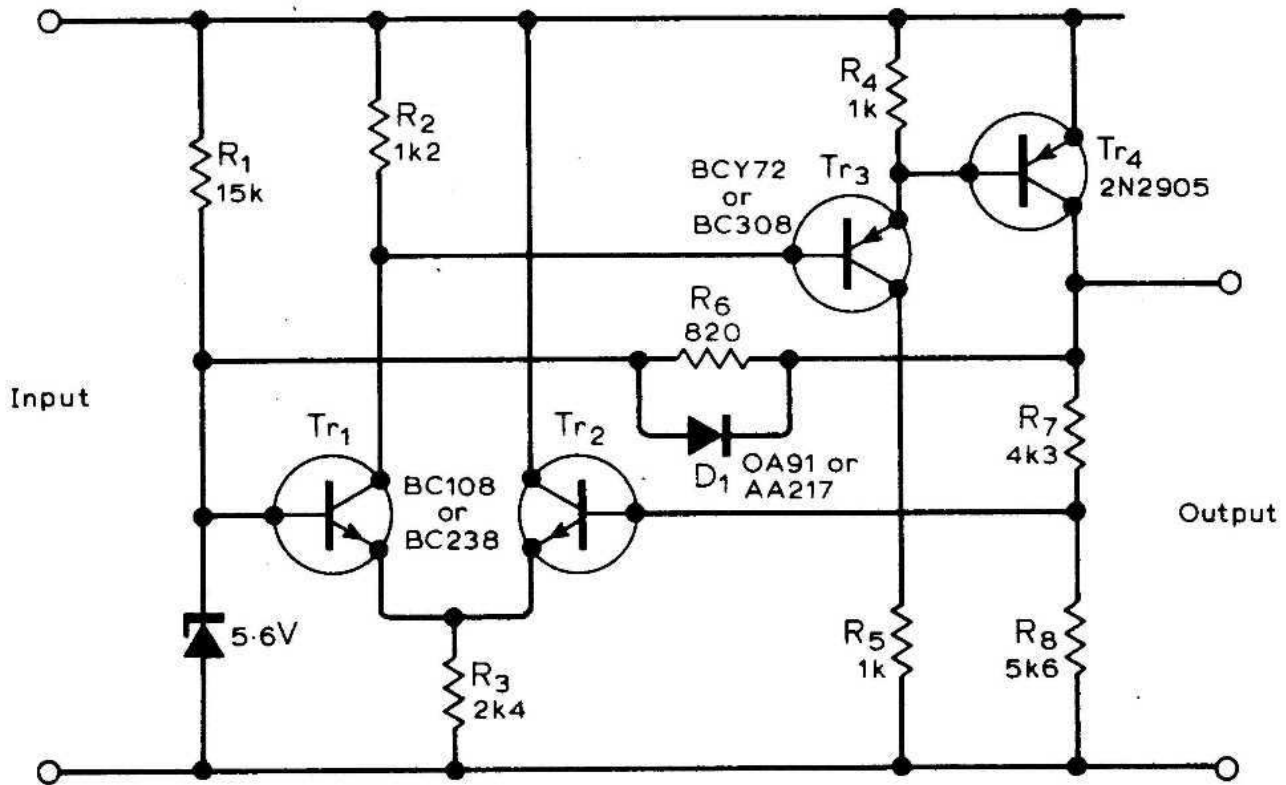

### Germanium diode for regulator protection

Power regulator protection is a perennial problem and this circuit offers a simple and economical solution. Under normal conditions, D1 is reverse biased by the voltage across R6 and does not affect the regulator operation. When the output is shorted, however, D1 turns on and draws current through R6, which removes the reference voltage across the zener diode. Because D1 is a germanium type, Tr1 is held off which also turns Tr3 and Tr4 off. When the short is removed, the circuit recovers and resumes normal operation.


D. E. O'N. Waddington, St Albans, Herts.

Wireless World, March 1977

(Continued on page 7)

# A Collection of Circuit Ideas - 1

(Continued from page 6)

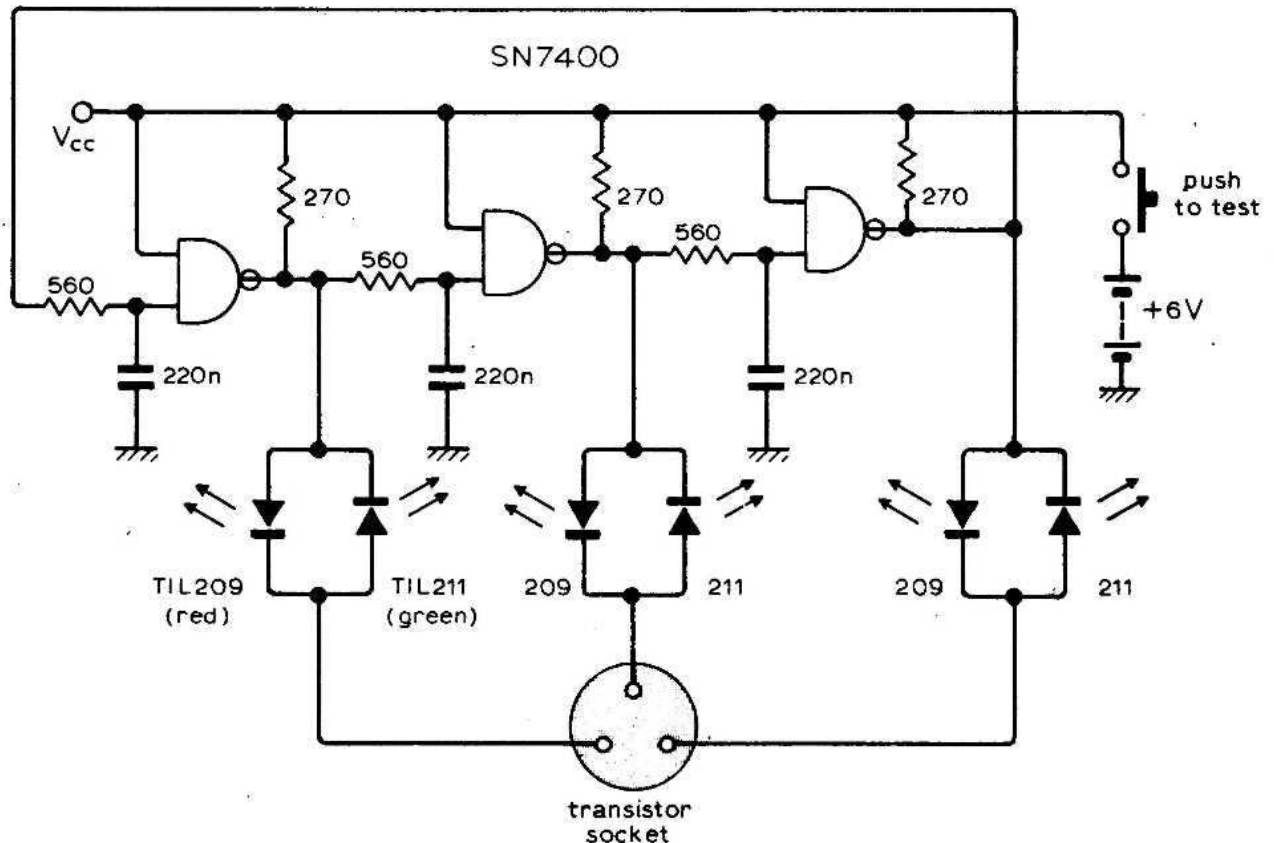

## Semiconductor tester

This circuit tests transistors and diodes for polarity, and short/open circuits in one measurement. The same tests using a multimeter would require at least four operations.


A three-phase waveform is derived from the low-frequency ring-of-three oscillator, and applied to the device under test via the L.e.d.s. The oscillator waveform enables each pair of device terminals to be forward, reverse and unbiased for one third of a cycle.

Current flowing into the device will turn the appropriate red L.e.d. on and current flowing out will turn on the green L.e.d. Thus, the position of the base lead and the polarity of a transistor may be deduced.

Voltage drop across the l.e.d.'s and device under test is typically 4.5V. A t.t.l. "1" will not source current at this voltage, so 270 Ohm resistors have been added to source and limit the diode current. Frequency of operation, defined by the CR network, is not critical, but the resistor should not exceed 1k2 for reliable operation. Oscillator frequency with the values shown is about 2 kHz.


N. E. Thomas, Balham, London.

(continued on page 8)

 

# A Collection of Circuit Ideas - 1

(continued from page 7)

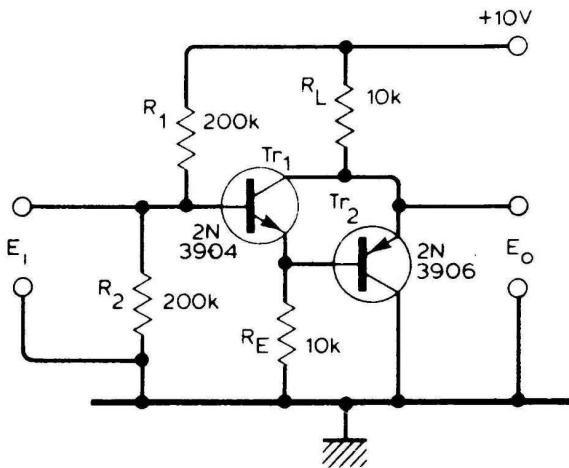

## Unity gain buffer with wide frequency response

By d.c. coupling a n-p-n. common emitter stage with a p-n-p emitter follower stage sharing a common load resistor, a unity gain buffer is formed which offers a high input impedance, wide frequency response, low output impedance and low current consumption.

The 3 dB bandwidth is above 80 MHz and by selecting better transistors this can be extended. Care in minimising the lead inductance and stray capacitance will also improve this figure.


Current consumption is about a mA with a 10V supply. The circuit will operate from 3 to 30V without degrading its performance. It is important to select the correct input biasing resistors because they reduce the input impedance.

A. L. Equizabal Vancouver Canada

## Variable power supply with zener stabilization

In regulated power supplies it is advantageous to feed the reference zener diode from the stabilized line. This is more difficult with a variable voltage supply; however, a simple solution to the problem is to use a dual linear potentiometer as in the circuit shown.

L. J. Baughan, Charlbury, Oxon.

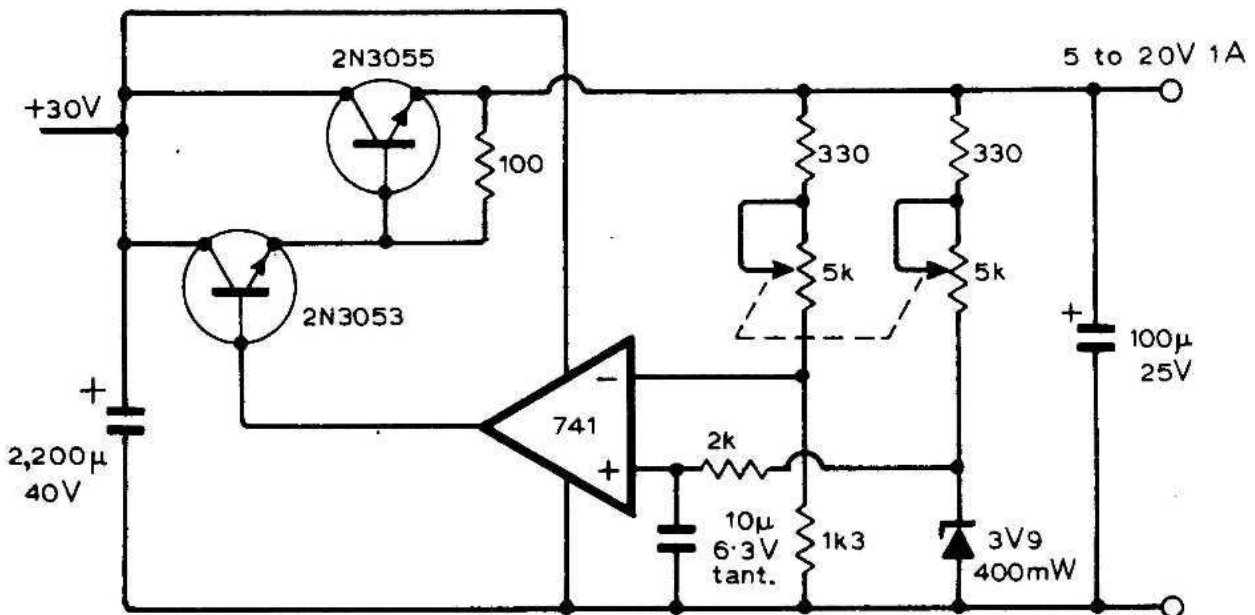



## Editor's Comments

*(Continued from page 1)*

"If you are a senior you will understand this one, if you deal with seniors this should help you understand them a little better, and if you are not a senior yet.....God willing, someday you will be.....

### **The \$2.99 Special**

We went to breakfast at a restaurant where the 'seniors' special' was two eggs, bacon, hash browns and toast for \$2.99.

'Sounds good,' my wife said.. 'But I don't want the eggs.'

'Then, I'll have to charge you three dollars and forty-nine cents because you're ordering a la carte,' the waitress warned her.

'You mean I'd have to pay for not taking the eggs?' my wife asked incredulously.

'YES!!' stated the waitress.

'I'll take the special then,' my wife said.

'How do you want your eggs?' the waitress asked.

'Raw and in the shell,' my wife replied. She took the two eggs home and baked a cake.

**DON'T MESS WITH SENIORS!!!**

**WE'VE been around the block more than once!"**

JB 2009-11-08

**The West Rand Amateur Radio Club**

Established in 1948

KG33XU 26.14122 South - 27.91870 East

P.O. Box 562  
Roodepoort  
1725

**Phone: 082 342 3280** (Chairman)

**Email: [zs6wr.club@gmail.com](mailto:zs6wr.club@gmail.com)**

**Web page: [www.jbcs.co.za/ham\\_radio](http://www.jbcs.co.za/ham_radio)**

**Bulletins** (Sundays at ...)

11h15 Start of call in of stations

11h30 Main bulletin start

**Frequencies**

439.000MHz 7.6MHz split

Input: 431.4MHz (West Rand Repeater)

145,625 MHz (West Rand Repeater)

10,135 MHz (HF Relay)

**Radio Amateurs do it with more frequency!**


Chairman	Joop Hesp	ZS6C	082 342 3280	<a href="mailto:zs6wr.club@gmail.com">zs6wr.club@gmail.com</a> <b>OR</b> <a href="mailto:joophesp@telkomsa.net">joophesp@telkomsa.net</a>
Vice Chairman	Geoff	ZS6GRL	082 546 5546	<a href="mailto:glevey@gmail.com">glevey@gmail.com</a>
Secretary	Phillip	ZS6PVT	083 267 3835	<a href="mailto:phillipvt@sse.co.za">phillipvt@sse.co.za</a>
Treasurer	Craig Woods	ZS6CRW	082 700 0163	<a href="mailto:craig.woods@absamail.co.za">craig.woods@absamail.co.za</a>
Member	Romeo Nardini	ZS6ARQ	082 552 4440	<a href="mailto:roshelec@global.co.za">roshelec@global.co.za</a>
Member (Anode)	John Brock	'PieRat'	011 768 1626	<a href="mailto:brockjk@gmail.com">brockjk@gmail.com</a>
Member (Technical)	Ron	ZR6RON	082 902 8343	<a href="mailto:ronnie@calidus.co.za">ronnie@calidus.co.za</a>
SARL Liaison	Willem	ZS6WWJ	082 890 6775	<a href="mailto:marie.w@absamail.co.za">marie.w@absamail.co.za</a>

**West Rand members - we need your input!**

To make this the best ham radio magazine in South Africa we need your input. Please submit articles, comments, suggestions etc.

Please send plain text with no formatting to the email address below.

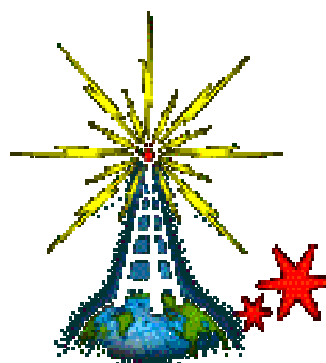In July 2003, we re-published an Anode Compendium on CD. It has the issues from July 2000 until June 2005. This included the new Adobe reader. It has been updated, check with the chairman for details.



**We need your input! Email us articles, comments and suggestions please.**  
[zs6wr.club@gmail.com](mailto:zs6wr.club@gmail.com)